

## Exp No.: 03

### Name of the Experiment:

Design and Observation of CMOS Characteristics for **NAND** and **NOR** Gates

### Theory


A CMOS logic gate is formed by a complementary pair of networks: a **pull-down network (PDN)** of nMOS devices that conducts for output 0, and a **pull-up network (PUN)** of pMOS devices that conducts for output 1. Series connections realize logical AND; parallel connections realize logical OR. The PUN is the dual of the PDN.

#### CMOS 2-input NAND

The Boolean function is

$$Y_{\text{NAND}} = \overline{A \cdot B}$$

 - **PDN (nMOS):** devices for  $A$  and  $B$  **in series** implement  $A \cdot B$ .
- **PUN (pMOS):** devices for  $A$  and  $B$  **in parallel** implement  $\bar{A} + \bar{B}$ .  
The output only falls when both inputs are high; for any other combination, at least one pMOS is on and the output is held high.




#### CMOS 2-input NOR

The Boolean function is

$$Y_{\text{NOR}} = \overline{A + B}$$

 - **PDN (nMOS):** devices for  $A$  and  $B$  **in parallel** implement  $A + B$ .
- **PUN (pMOS):** devices for  $A$  and  $B$  **in series** implement  $\bar{A} \cdot \bar{B}$ .  
The output only rises when both inputs are low; otherwise at least one nMOS pulls it down.



### Truth Tables


A	B	$Y_{\text{NAND}}$	$Y_{\text{NOR}}$
0	0	1	1
0	1	1	0
1	0	1	0
1	1	0	0

Key expectations include rail-to-rail swings, negligible static power, and propagation delay dominated by the longest conducting series path (NAND worst-case fall; NOR worst-case rise).


## Required Tools

- **MICROWIND** – CMOS layout and analog simulation
- **DSCH** – schematic / logic capture (optional)
- **Word Processor** – documentation

## Circuit Diagram

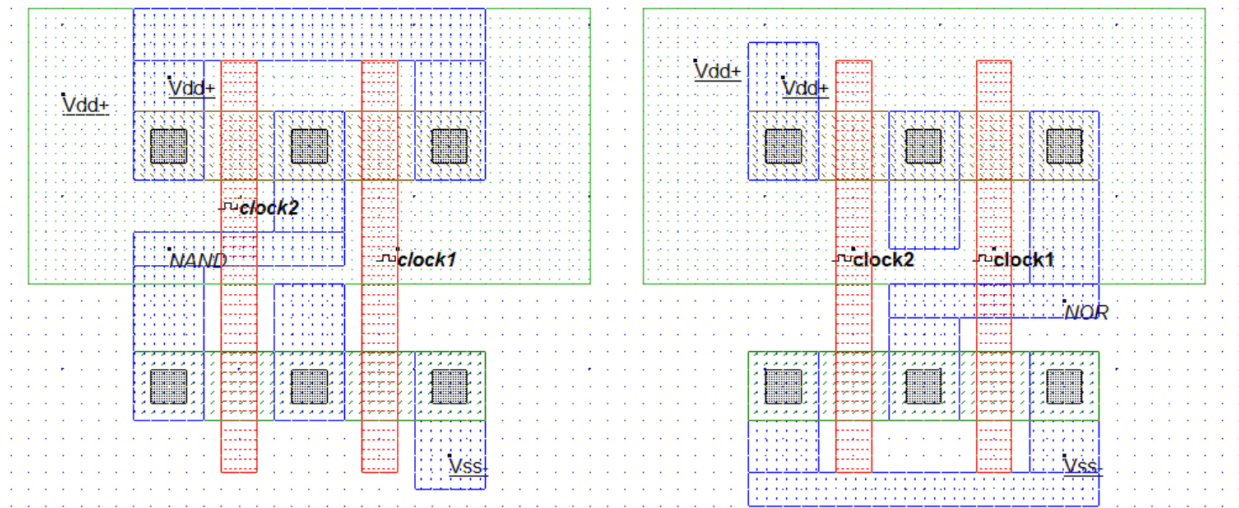

## Output

 

## Results

Inputs were driven by two clocks (**clock1**, **clock2**). The displayed supply rail was approximately **1.2 V**, time scale **2 ns/div**, and simulation **step = 0.1 ps**.

- **NAND output:** stayed high except when both inputs were high, when it transitioned low—consistent with  $\overline{A \cdot B}$ . Measured propagation-delay annotations on edges were around **3–10 ps** depending on direction and input vector ordering.
- **NOR output:** stayed low except when both inputs were low, when it transitioned high—consistent with  $\overline{A + B}$ . Delay markers indicated **~1–6 ps** on the shown events.
- The simulator's power readout indicated  $P \approx 4.222 \mu\text{W}$  average under the applied toggling activity.

These observations match the theoretical truth tables and the dual series/parallel topology of CMOS NAND/NOR.

## Discussion & Conclusion

The NAND and NOR gates were realized with complementary CMOS pull-up and pull-down networks and verified in transient simulation. The outputs exhibited correct logic behavior with rail-to-rail levels, while measured delays ( $\approx 1\text{--}10$  ps) reflected the expected dependence on transistor stacking: the NAND's worst-case fall delay was larger due to series nMOS, and the NOR's worst-case rise delay was larger due to series pMOS. The reported average power of about  $4.2 \mu\text{W}$  confirmed low dynamic consumption and negligible static current. Hence, the CMOS implementations satisfied functional correctness and demonstrated characteristic delay asymmetries inherent to NAND/NOR structures.

## References

1. R. J. Baker, *CMOS: Circuit Design, Layout, and Simulation*, Wiley-IEEE.
2. N. H. E. Weste and D. Harris, *CMOS VLSI Design: A Circuits and Systems Perspective*, Addison-Wesley.
3. MICROWIND/DSCH User Manuals, Microwind Inc.